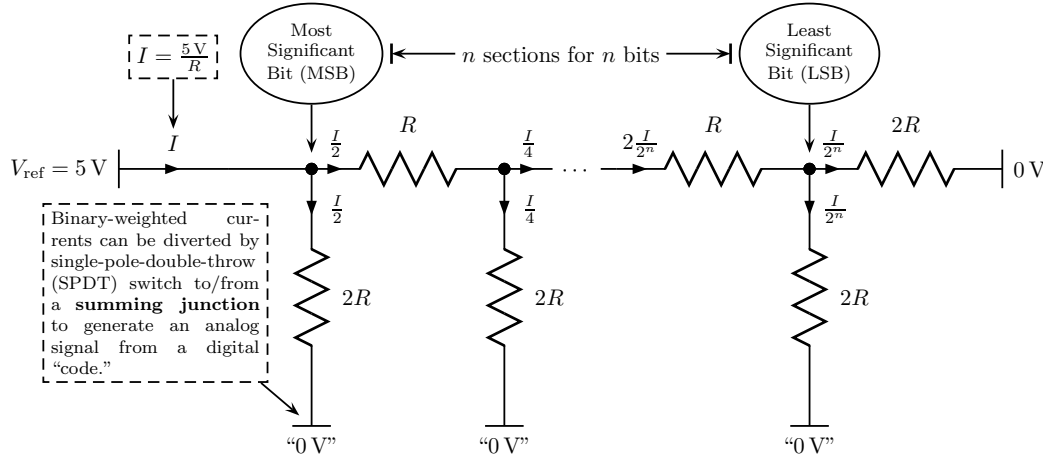


ECE 209: *Circuits and Electronics Laboratory*

Notes for Lab 7 (Digital-to-Analog (D/A) Application)

1. Digital-to-analog converter (DAC) — “1 least significant bit (LSB)” \triangleq *Smallest output step possible*

- Now, signals are generated by a computer as *codes* separated by intervals of time.
- To use those signals in the physical world, need to convert those abstract codes to voltages.
- When codes are in binary, each bit can *electronically* control a switch (e.g., a *transistor*); those switches turn on and off currents into **summing junction** formed by operational amplifier.
 - Amplifier **gain** changes output *scale* — “clicking” heard in function generators (50 Ω output?).
 - Modern DAC’s use more complicated schemes. “1-bit DAC” technologies *pulse* modulate.
 - * *Switches* (as opposed to analog amp.) burn negligible power (wall switches vs. dimmers).
 - * Increase “number of bits” by increasing samples per second (no extra hardware).
 - * So adjusting intensity in **time** can be very efficient and very cheap to implement.
 - * Example: Digital lights only need to *quickly* turn red/green/blue on/off independently.
- The standard summing amplifier uses weighted resistances to generate different currents.
 - In the configuration shown in the book, every new code causes current from V_{ref} to change.
 - * Rapidly changing current can cause noise to spread to far regions of a circuit.
 - * To fix, change pre-resistor **SPST** to post-resistor **SPDT** between ground & **virtual ground**.
 - More importantly, *integrated circuit* resistance *matching* is easy, but *ratio matching* is difficult.
 - * Greatly affects *linearity* of the DAC (see **INL/DNL** nonlinearity specifications).
- Clever R - $2R$ ladder solves both problems
 - Equivalent resistance into each ladder “wrung” is R (i.e., (new wrung)||ladder = $2R$ ||($R+R$)).
 - Regardless of number of bits and switch state, current into ladder is a fairly steady V_{ref}/R .
 - Each new section halves previous current. Last wrung of n -bit DAC carries $V_{\text{ref}}/R \times 2^{-n}$.



2. Introduce and complete the *Digital-to-Analog (D/A) Application* lab.

- Resistor color codes: Black, Brown, ROYGBV, Gray, White correspond to **digits** 0–9
 - **Brn-Blk-Red**: 1 k Ω , **Brn-Red-Red**: 1.2 k Ω , **Red-Red-Red**: 2.2 k Ω , **Brn-Blk-Orange**: 10 k Ω
 - Also try parallel or series combinations (note: only R_F/R_0 and R_F/R **ratios** matter)
 - * A resistance R is equal to $2R$ in parallel with $2R$ (e.g., 5 k Ω = 10 k Ω ||10 k Ω).
- Mimic switches by **manually** connecting and disconnecting wires (don’t open-circuit R - $2R$!).
- For V_{ref} , use **sine wave** @ 5 V_{RMS} & 1 kHz; set DVM for $V_{\text{RMS,AC}}$ (expect **positive** values).